

## Logic Design Basics

From Prof. Joongnam Jeon's lecture slides

# 3.1 Logics

---

Logics: a math of truth values

Logic Value

Logic Value	거짓(false)	참(true)
Binary	0	1
Switch	닫힘(off)	열림(on)
Signal	끊김(Low)	흐름(High)

Constants = {false, true} = {0, 1}

Propositional variables. Ex) x, y, z, a1, a2, alarm, bell

- Input variables
- Output variables

A logic formula defines the relation of input and output variables

# Logic Representations

Three Representations: Truth Table, Logic Formula, Logic Circuit

Truth table

Input variables	Output variables
Combinations of input values	Expected outputs for each input case

Ex. Even or Not

x	y	z	F
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

# Primitive Logic Operations

---

AND $Z = X \cdot Y = XY = X \text{ AND } Y = X \wedge Y$		
X	Y	Z
0	0	0
0	1	0
1	0	0
1	1	1

OR $Z = X + Y = X \text{ OR } Y = X \vee Y$		
X	Y	Z
0	0	0
0	1	1
1	0	1
1	1	1

NOT $Z = \overline{X} = X' = \neg X$	
X	Z
0	1
1	0

# 3.2.1 Boolean Algebra

---

## Algebra

- Axioms
- Set
- Operations
- Equations

## Operations

- Binary operator
  - With Real numbers:  $+$ ,  $-$ ,  $\times$ ,  $\div$
  - With Boolean numbers: AND, OR
- Unary operator
  - With real number: negation, square root, log
  - With Boolean number: NOT

# Boolean Algebra

---

Named after George Boole, 1815-1864

Boolean algebra

- Elements =  $\{0, 1\}$
- Operators =  $\{\text{AND}(\cdot), \text{OR}(+), \text{NOT}(')\}$

The result of every Boolean operation is a Boolean value

Dual equation

- $x \wedge x = x$
- $x \wedge 0 = 0$
- $\neg(\neg x) = x$
- $x \vee x = x$
- $x \vee 1 = 1$

# Properties of Boolean Algebra

---

- Associative Law

- $(x \vee y) \vee z = x \vee (y \vee z)$
- $(x \wedge y) \wedge z = x \wedge (y \wedge z)$

- Commutative Law

- $x \vee y = y \vee x$
- $x \wedge y = y \wedge x$

- Distributive Law

- $x \vee (y \wedge z) = (x \vee y) \wedge (x \vee z)$
- $x \wedge (y \vee z) = (x \wedge y) \vee (x \wedge z)$

# Identity and Complement

---

- Identity elements

- $x \vee 1 = 1$
- $x \wedge 0 = 0$

- Complements

- $x \vee \neg x = 1$
- $x \wedge \neg x = 0$



# Proof of Boolean Statement

Using Truth Table

$$x \bullet (y + z) = (x \bullet y) + (x \bullet z)$$

$$x \wedge (y \vee z) = (x \wedge y) \vee (x \wedge z)$$

Atomic Propositions			Left-hand side		Right-hand sides		
x	y	z	$y \vee z$	$x \wedge (y \vee z)$	$(x \wedge y)$	$(x \wedge z)$	$(x \wedge y) \vee (x \wedge z)$
0	0	0					
0	0	1					
0	1	0					
0	1	1					
1	0	0					
1	0	1					
1	1	0					
1	1	1					

# De Morgan's law

---


$$\neg(x \vee y) = \neg x \wedge \neg y$$

$$\neg(x \wedge y) = \neg x \vee \neg y$$


Atomic Propositions		Left-hand sides		Right-hand side		
x	y	$x \vee y$	$\neg(x \vee y)$	$\neg x$	$\neg y$	$\neg x \wedge \neg y$
0	0					
0	1					
1	0					
1	1					

## 3.3.1 Basic Logic Gates

### Electrical Components for Boolean Logic Operations

 


[그림 3-1] 논리게이트 기호

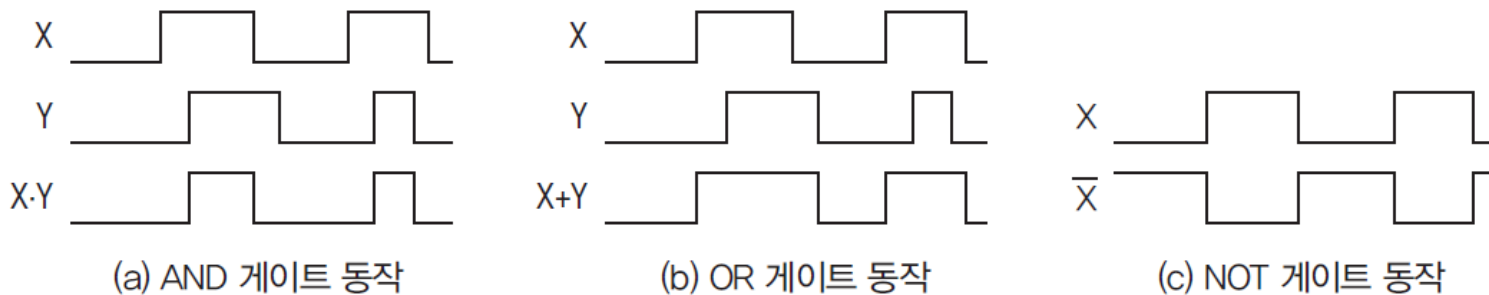


[그림 3-2] 기본 게이트의 출력에 대한 타이밍 다이어그램
 
# Propagation Delay

- Time duration between an input signal change and the output signal change
  - mostly, in few nanoseconds
- Delay gets cumulated as a signal passes through multiple logic gates




(a) AND 게이트의 전파 시간

 


(b) 논리회로의 출력 지연

[그림 3-3] 전파 지연

# Power Supply and Fan-out

 


(a) 트랜지스터 AND 게이트

 

(b) 팬아웃(fan-out)

[그림 3-4] 전원 공급과 팬아웃

### 3.3.3 Logic Gate Notation

 


[그림 3-6] 제어선과 신호선




(a) 삼각형



(b) 작은 원

 

(c) 직선형 입력

 

(d) 곡선형 입력

[그림 3-7] 논리게이트 표현 기호

신호 전달



신호 부정(NOT)  
입력/출력에 추가

AND 연산  
입력선 2개 이상



OR 연산  
입력선 2개 이상

## 3.3.4 AND and NAND

〈표 3-7〉 2-입력 AND 게이트



입력		출력	AND 게이트 기호	
X	y	$F = x \cdot y$	입력 정논리 - 출력 정논리	입력 부논리 - 출력 부논리
0	0	0		
0	1	0		
1	0	0		
1	1	1		

〈표 3-8〉 2-입력 NAND 게이트



입력		출력	NAND 게이트 기호	
X	y	$F = (x \cdot y)'$	입력 정논리 - 출력 부논리	입력 부논리 - 출력 정논리
0	0	1		
0	1	1		
1	0	1		
1	1	0		

# OR and NOR

〈표 3-9〉 2-입력 OR 게이트

입력		출력	OR 게이트 기호	
X	y	$F = x+y$	입력 정논리 - 출력 정논리	입력 부논리 - 출력 부논리
0	0	0		
0	1	1		
1	0	1		
1	1	1		


〈표 3-10〉 2-입력 NOR 게이트

입력		출력	NOR 게이트 기호	
x	y	$F = (x+y)'$	입력 정논리 - 출력 부논리	입력 부논리 - 출력 정논리
0	0	1		
0	1	0		
1	0	0		
1	1	0		




# XOR and XNOR

〈표 3-11〉 2-입력 XOR 게이트

입력		출력	XOR 게이트 기호
X	y	$F=x\oplus y$	
0	0	0	
0	1	1	
1	0	1	
1	1	0	


〈표 3-12〉 2-입력 XNOR 게이트

입력		출력	XNOR 게이트 기호
x	y	$F=(x\oplus y)'$	
0	0	1	
0	1	0	
1	0	0	
1	1	1	

# Buffer, Not, 3-in Gates



(a) 버퍼

 

(b) 정논리 NOT 게이트



(c) 부논리 NOT 게이트

[그림 3-8] 버퍼와 NOT 게이트



(a)  $F = X \cdot Y \cdot Z$



(b)  $F = X + Y + Z$



(c)  $F = X \oplus Y \oplus Z$



(d)  $F = (X \cdot Y \cdot Z)'$



(e)  $F = (X + Y + Z)'$



(f)  $F = (X \oplus Y \oplus Z)'$

[그림 3-9] 3-입력 게이트