


Combinatorial Logic

from Prof. Joongnam Jeon's lecture slides

Combinatorial Logic Circuit

Combinational logic circuit

- the output of a combinatorial logic circuit is completely determined by given input values

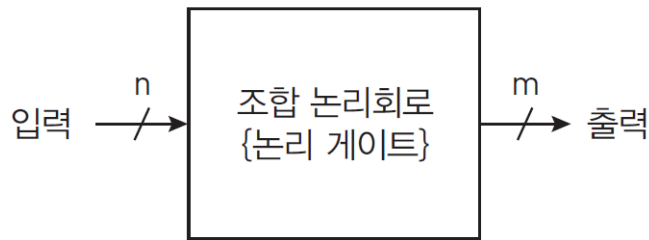

[그림 4-1] $n \times m$ 조합 논리회로

Table 4-1. $m \times n$ combinatorial logic circuit

No.	Input				Output			
	X_n	X_{n-1}	...	X_1	Y_m	Y_{m-1}	...	Y_1
0	0	0	0	0				
1	0	0	0	1				
2	0	0	1	0				
...								
2^n-1	1	1	1	1				

Logic Equation to Logic Circuit


Precedence order

- OR < AND < NOT < Parentheses

Drawing Logic Circuit Diagram

1. Place input signals at the left-side, output signals at the right-side
2. Draw logic gates and connect their input and outputs considering precedence order

Ex. $F = x \cdot y + x' \cdot z$

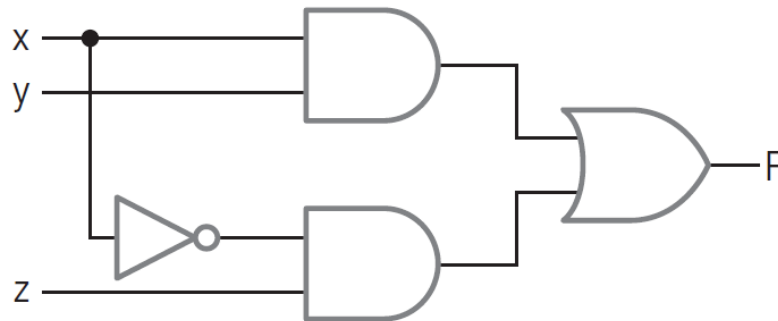

Minterms

Generate logic formula from truth table

- sum of products
 - examples
 - $F1(x,y,z) = x + y \cdot z$
 - $F2(x,y,z) = x \cdot y + x' \cdot z$
 - $F3(x,y,z) = x' \cdot y' \cdot z' + x \cdot y \cdot z$
- products of sums

Minterm: a product where each variable (or its negative) is connected as an operand

- a minterm evaluates to True only with one combination of input values
- ex. for three input variables x, y, z ,
 - minterms: $x'y'z'$, $x'yz$, $xy'z$, etc.

Minterms

Input			Minterms							
x	y	z	m_0 $x'y'z'$	m_1 $x'y'z$	m_2 $x'yz'$	m_3 $x'yz$	m_4 $xy'z'$	m_5 $xy'z$	m_6 xyz'	m_7 xyz
0	0	0								
0	0	1								
0	1	0								
0	1	1								
1	0	0								
1	0	1								
1	1	0								
1	1	1								

Sum of Minterms

x	y	z	F	m ₁	m ₃	m ₆	m ₇
0	0	0	0				
0	0	1	1				
0	1	0	0				
0	1	1	1				
1	0	0	0				
1	0	1	0				
1	1	0	1				
1	1	1	1				

(1) Sum of Minterms


$F(x,y,z) =$ _____

(2) Simplified Formula

$F(x,y,z) =$ _____

7-Segment Display


8421 BCD 7-segment Display Decoder

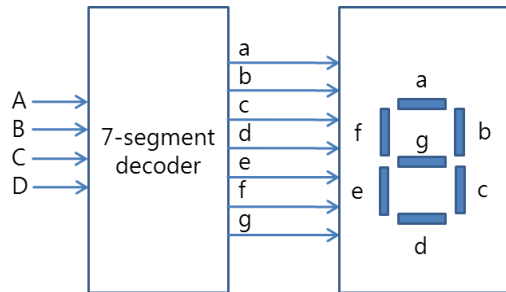

Hex. No	A	B	C	D	a	b	c	d	e	f	g
0	0	0	0	0	1	1	1	1	1	1	0
1	0	0	0	1							
2	0	0	1	0							
3	0	0	1	1							
4	0	1	0	0							
5	0	1	0	1							
6	0	1	1	0							
7	0	1	1	1							
8	1	0	0	0							
9	1	0	0	1							
A	1	0	1	0	X	X	X	X	X	X	X
B	1	0	1	1	X	X	X	X	X	X	X
C	1	1	0	0	X	X	X	X	X	X	X
D	1	1	0	1	X	X	X	X	X	X	X
E	1	1	1	0	X	X	X	X	X	X	X
F	1	1	1	1	X	X	X	X	X	X	X

- X: Don't care

Adder

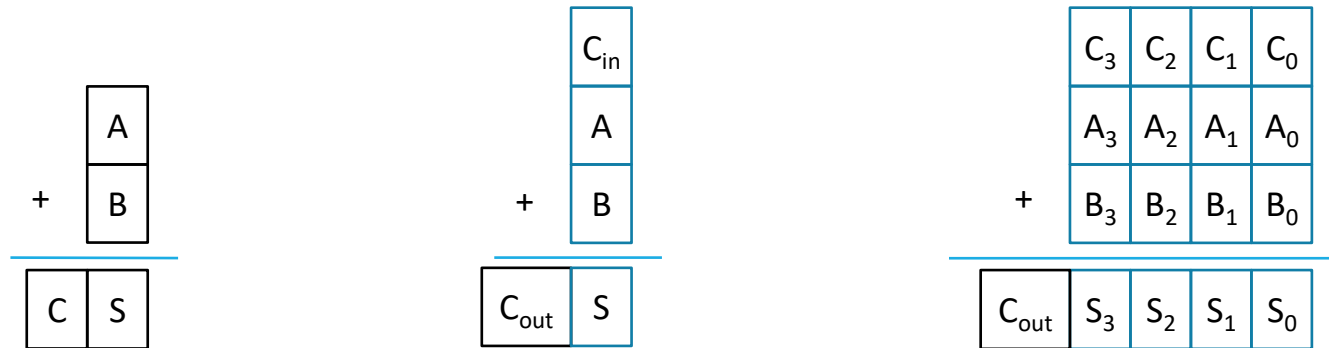

(a) Half adder

(b) Full adder

(c) 4-bit Adder

Half Adder

- Input: A, B
- Output: S(sum), C(carry)
- Truth Table


Input		Output		Note
A	B	C	S	
0	0			$0 + 0 = 00$
0	1			$0 + 1 = 01$
1	0			$1 + 0 = 01$
1	1			$1 + 1 = 10$

Logic Formula

$S =$ _____

$C =$ _____

Logic Circuit

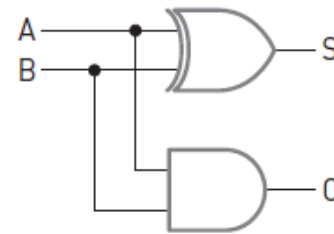

(a) 논리회로도



(b) 블록도

Full Adder

- Input: A, B, C_{in} (carry in)
- Output: S (sum), C_{out} (carry out)
- Truth Table


Input			Output		Note
A	B	C_{in}	C_{out}	S	
0	0	0			$0 + 0 + 0 = 00$
0	0	1			$0 + 0 + 1 = 01$
0	1	0			$0 + 1 + 0 = 01$
0	1	1			$0 + 1 + 1 = 10$
1	0	0			$1 + 0 + 0 = 01$
1	0	1			$1 + 0 + 1 = 10$
1	1	0			$1 + 1 + 0 = 10$
1	1	1			$1 + 1 + 1 = 11$

Full Adder


Logic Formula

- $S = A \oplus B \oplus C_{in} = (A \oplus B) \oplus C_{in}$
- $C_{out}(\text{carry out}) = A \cdot B + B \cdot C_{in} = A \cdot B + (A \oplus B) \cdot C_{in}$

Logic Circuit

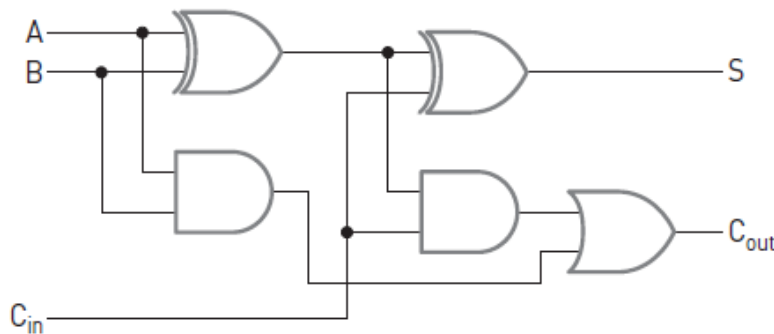


(a) 반가산기 2개와 OR 게이트로 구현

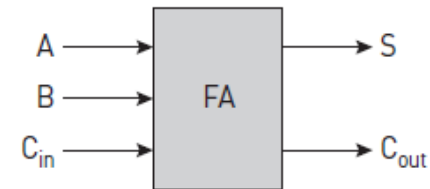

(b) 블록도

Parallel Adder

4-bit parallel adder

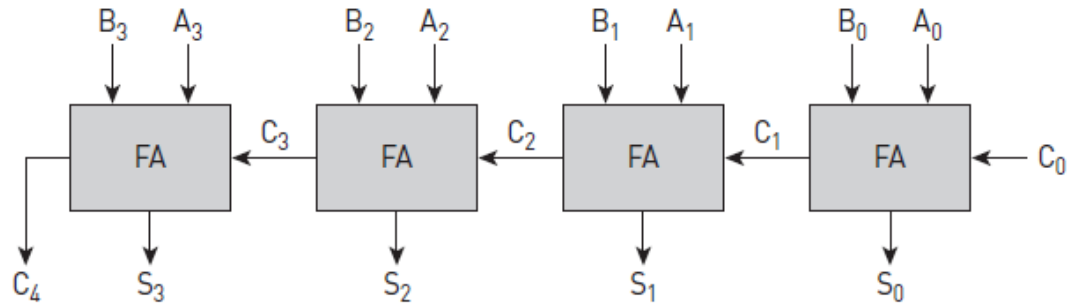


Ex. $C_0=0$, $X=0011$, $Y=1110$

X:	0 0 1 1
Y:	<u>1 1 1 0</u>
S:	
C:	

Comparator

Input and output

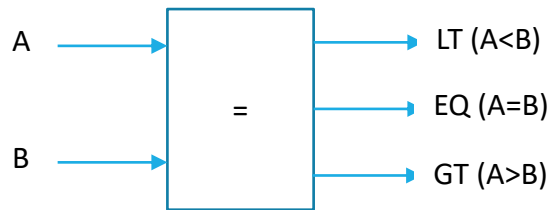

Logic Formula

$$LT = \underline{\hspace{2cm}} // A=0, B=1$$


$$GT = \underline{\hspace{2cm}} // A=1, B=0$$

$$EQ = \underline{\hspace{2cm}} // AB = 00 \text{ or } 11$$
$$= (LT + GT)'$$

Truth table

Input		Output			Note
A	B	LT	EQ	GT	
0	0				0 = 0
0	1				0 < 1
1	0				1 > 0
1	1				1 = 1


Logic Circuit

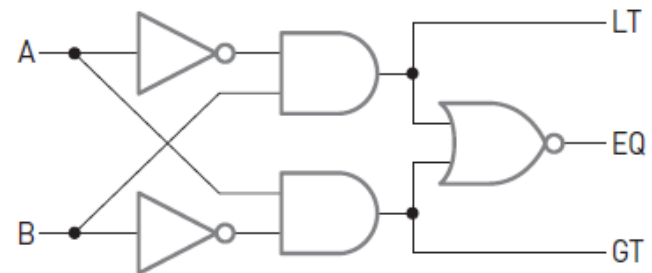

4-bit Comparator

Compare two 4-bit numbers: either GT, EQ, LT

입력		출력			비고
$A_3A_2A_1A_0$	$B_3B_2B_1B_0$	LT	EQ	GT	
$X_3X_2X_10$	$X_3X_2X_11$				A < B
$X_3X_20\text{ d}$	$X_3X_21\text{ d}$				
$X_30\text{ d d}$	$X_31\text{ d d}$				
0 d d d	1 d d d				
$X_3X_2X_1X_0$	$X_3X_2X_1X_0$				A = B
$X_3X_2X_11$	$X_3X_2X_10$				A > B
$X_3X_21\text{ d}$	$X_3X_20\text{ d}$				
$X_31\text{ d d}$	$X_30\text{ d d}$				
1 d d d	0 d d d				

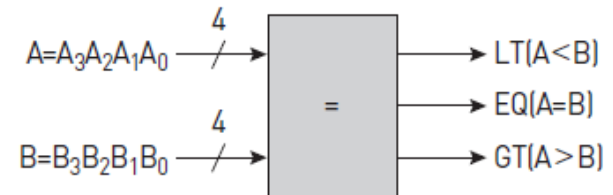

Example

1) A = 1010, B = 1001
LT=__, EQ=__, GT=__

2) A = 0101, B = 0101
LT=__, EQ=__, GT=__

3) A = 0001, B = 0010
LT=__, EQ=__, GT=__