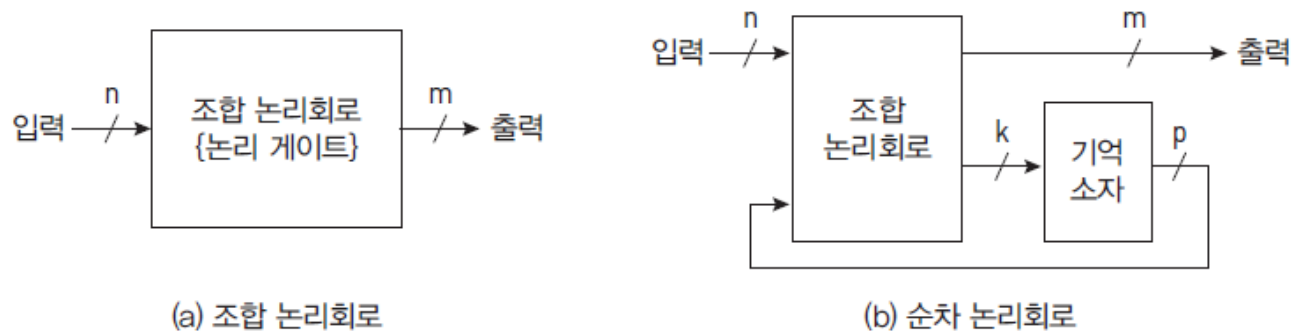


Sequential Logic System

From Prof. Joongnam Jeon's lecture slides

Sequential Logic System



[그림 6-1] 조합 논리회로와 순차 논리회로

Combinatorial Logic

- $\text{output} = f(\text{input})$

Sequential logic

- $\text{output, state} = f(\text{input, state})$



Synchronous Sequential Logic

Synchronous and Asynchronous Digital System

- Synchronous: all flip-flops share the same clock pulse
- Asynchronous: flip-flops do not share the same clock pulse


Synchronous Digital System

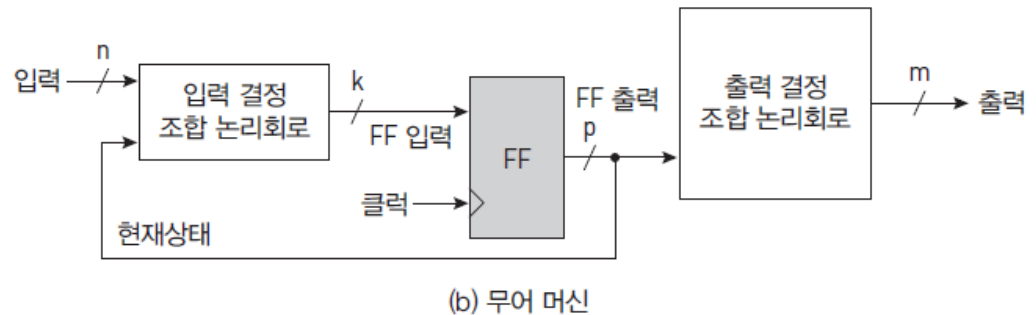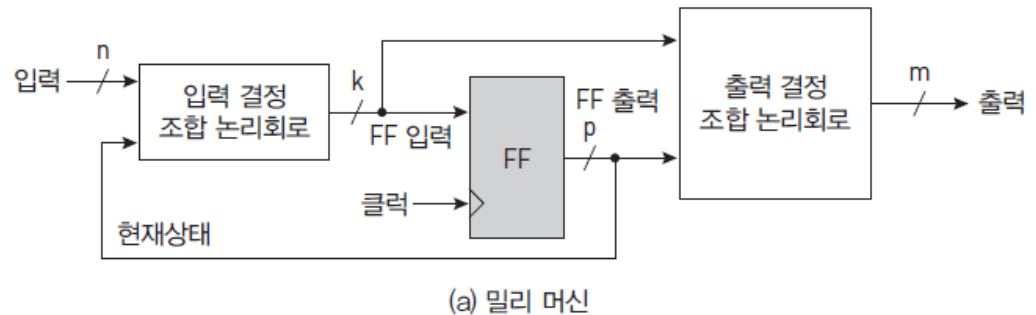- **Mealy machine**
 - $\text{output} = f(\text{input}, \text{state})$
 - $\text{state} = f(\text{input}, \text{state})$
- **Moore machine**
 - $\text{output} = f(\text{state})$
 - $\text{state} = f(\text{input}, \text{state})$




Temporal Behaviors

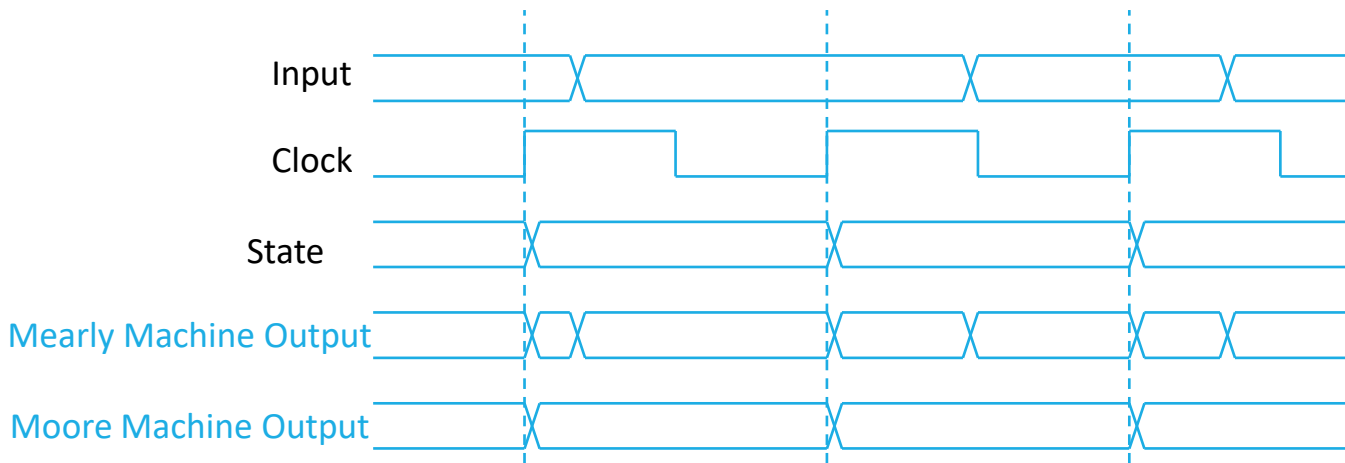- Mealy machine
 - $\text{output} = f(\text{input}, \text{state})$
 - $\text{state} = f(\text{input}, \text{state})$
- Moore machine
 - $\text{output} = f(\text{state})$
 - $\text{state} = f(\text{input}, \text{state})$
 - most digital systems are designed as Moore machines




Representing Moore Machine

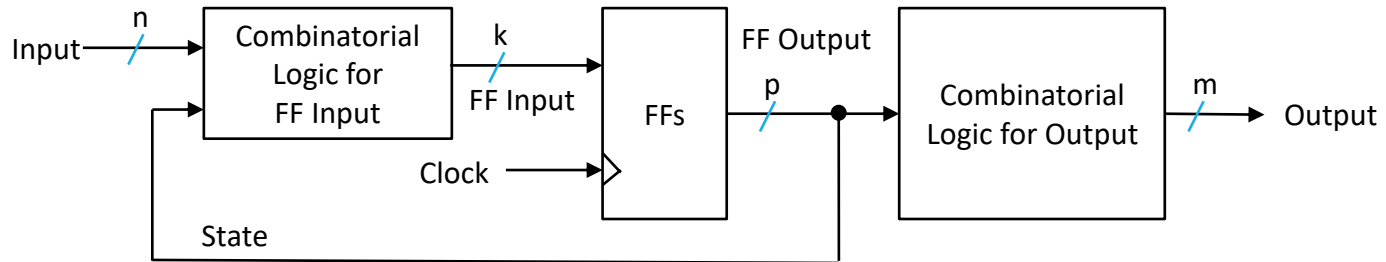

State diagram


상태 수 = 2^p

 

State table

	State	Input	State'	Output
$2^{(n+p)}$



Example

 

State	Input (X)	State*	Output (Y)
S_0	0	S_0	0
S_0	1	S_1	1
S_1	0	S_1	1
S_1	1	S_0	0

2-Input Sequence Detector

상태/출력	조건	비고
$S_0/0$	출력 1일 때 0이 연속해서 두 번 입력된 상태	초기상태
$S_1/0$	출력 0일 때 1이 한번 입력된 상태	
$S_2/1$	출력 0일 때 1이 연속해서 두 번 입력된 상태	
$S_3/1$	출력 1일 때 0이 한번 입력된 상태	

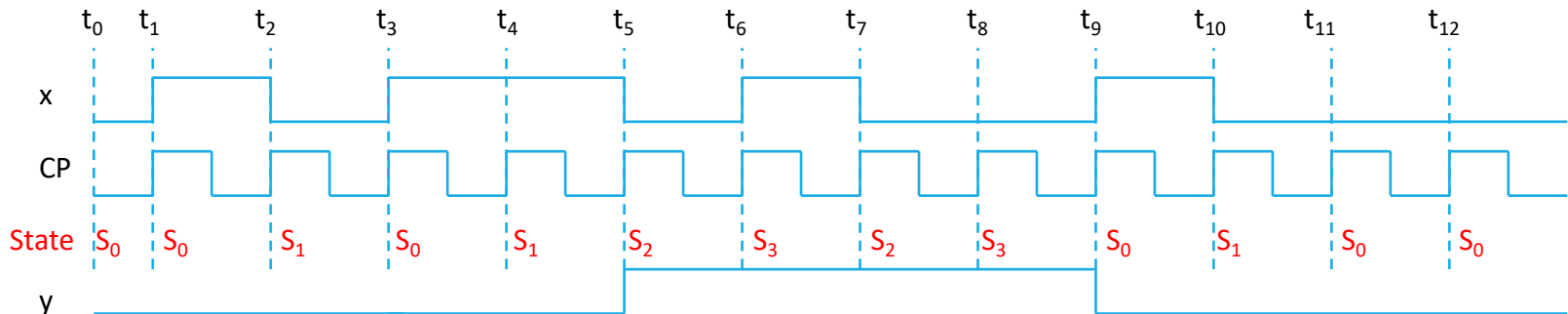 

< 2-입력 검출기의 동작 예 (상태 표시) >

Sequence Detector

- A sequence detector determines whether a specific sequence of input is given


- Each state represents the sequence pattern

- Example. 2-Input Detector


- detect whether the same

Current State		Output
State	Q_1 Q_0	y
S_0	0 0	0
S_1	0 1	0
S_2	1 0	1
S_3	1 1	1

Current State		Input	Next State	
State	Q_1 Q_0	x	State	Q_1 Q_0
S_0	0 0	0	S_0	0 0
S_0	0 0	1	S_1	0 1
S_1	0 1	0	S_0	0 0
S_1	0 1	1	S_2	1 0
S_2	1 0	0	S_3	1 1
S_2	1 0	1	S_2	1 0
S_3	1 1	0	S_0	0 0
S_3	1 1	1	S_2	1 0

 

Implementation with MUX


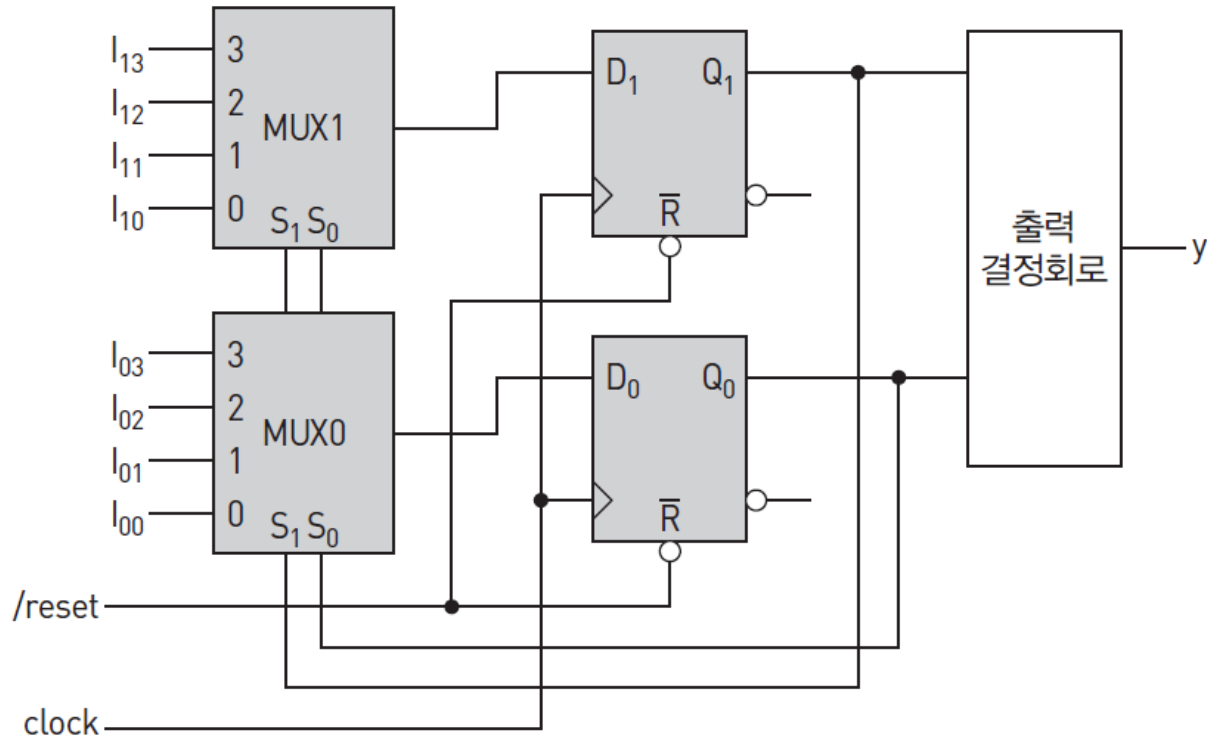


[그림 6-9] 멀티플렉서 구현의 일반 회로

Implementation with MUX

$Q_1 Q_0$	x	Q'_1	MUX1 In
00	0	0	0
00	1	0	
01	0	0	x
01	1	1	
10	0	1	1
10	1	1	
11	0	0	x
11	1	1	

$Q_1 Q_0$	x	Q^*_0	MUX0 In
00	0	0	x
00	1	1	
01	0	0	0
01	1	0	
10	0	1	x'
10	1	0	
11	0	0	0
11	1	0	

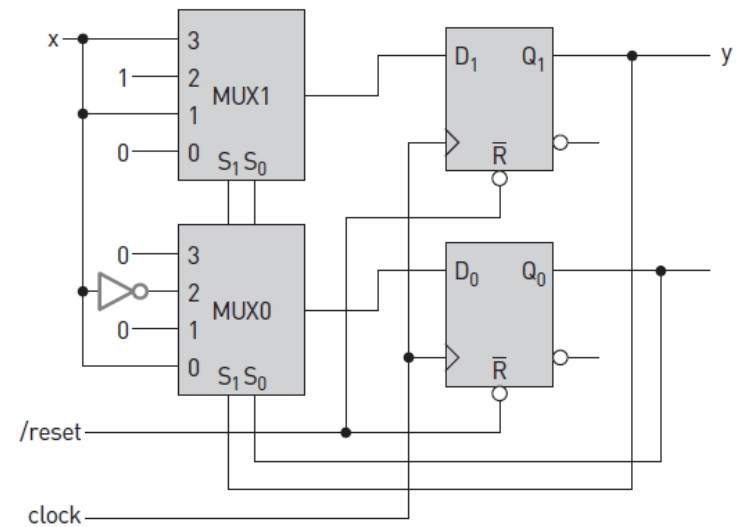 


[그림 6-10] 2-입력 검출기의 논리회로도


Example. 1-1-1 Detector

The output is one-bit indicating whether the last three input values were all one's.

State Diagram

 

Truth Table

 

Current State		Input	Next State	
State	$Q_1 Q_0$	x	State	$Q^*_1 Q^*_0$
S_0	0 0	0		
S_0	0 0	1		
S_1	0 1	0		
S_1	0 1	1		
S_2	1 0	0		
S_2	1 0	1		
S_3	1 1	0		
S_3	1 1	1		

Next State		Output
State	$Q^*_1 Q^*_0$	y

Combinatorial Logic Implementation with Two D Flip-flops

Current State		Input	Next State	
State	$Q_1 \ Q_0$	x	State	$Q^*_1 \ Q^*_0$
S_0	0 0	0		
S_0	0 0	1		
S_1	0 1	0		
S_1	0 1	1		
S_2	1 0	0		
S_2	1 0	1		
S_3	1 1	0		
S_3	1 1	1		

Next State		Output
State	$Q^*_1 \ Q^*_0$	y

MUX Implementation

현재상태 ($Q_1 Q_0$)	입력 (x)	다음상태 (Q^*_1)	MUX1 출력	현재상태 ($Q_1 Q_0$)	입력 (x)	다음상태 (Q^*_0)	MUX0 출력
S_0	0	0		S_0	0	0	
S_0	1	0		S_0	1	1	
S_1	0	0		S_1	0	0	
S_1	1	1		S_1	1	0	
S_2	0	0		S_2	0	0	
S_2	1	1		S_2	1	1	
S_3	0	0		S_3	0	0	
S_3	1	1		S_3	1	1	

MUX Implementation

